
 


## ELL201 – Tutorial Sheet 3

 1. A traffic signal cycles from GREEN to YELLOW, YELLOW to RED and RED to GREEN. In each cycle, GREEN is turned on for 70 seconds, YELLOW is turned on for 5 seconds and the RED is turned on for 75 seconds. This traffic light has to be implemented using a finite state machine (FSM). The only input to this FSM is a clock of 5 second period. What is the minimum number of flip-flops required to implement this FSM?
2. Design a Moore FSM that has output 'p' only if it receives a string of '01' on the serial input. Otherwise, the output will be 'q'. Convert the FSM to Mealy type.
3. Design a Mealy FSM that prints '1' when a string of 'aa' or 'bb' comes in the serial input line. Convert the FSM to Moore type.
4. The Finite state machine described by the following state diagram with A as starting state, where an arc label is  $x / y$  and  $x$  stands for 1-bit input and  $y$  stands for 2-bit output. Identify the function of the FSM.



5. Consider the following Mealy machine. Apply state reduction and answer the questions that follow.



- i. What is the number of states after reduction?

- ii. Mention any one pair of states that are equivalent.
- iii. Convert the reduced state machine from a Mealy Machine to a Moore Machine - How many states does it have?
- iv. During the above conversion from Mealy to Moore, mention any one state which undergoes a split into two states.
- v. Consider the FSM's initial state to be State D, and the Serial Input to the FSM be 11001101, what will be the output observed (8-bit)?